

CSE250

CIRCUITS AND ELECTRONICS

EXPERIMENT NO. : 02.....

EXPERIMENT NAME : INTRODUCTION TO SERIES
AND PARALLEL CIRCUITS.....

SHAIANE PREMA BAROI

ID: 21101098

SECTION: 07

1> Objective

The experiment is to acquaint the students with series-parallel circuits and to give them the idea about how to connect different circuits in bread board.

2> Apparatus

- DC power supplies
- resistors
- bread board
- multimeter

Proteus


- Battery
- Resistors
- Probes
- Connecting Wires
- Ground

3> Circuit / Block / System Diagram

objectives <

dtiw etasbuta sitf tnioupa at ei tnaemekse sitf
a(a) sit mnt evig of bao eniusitellorq-asina

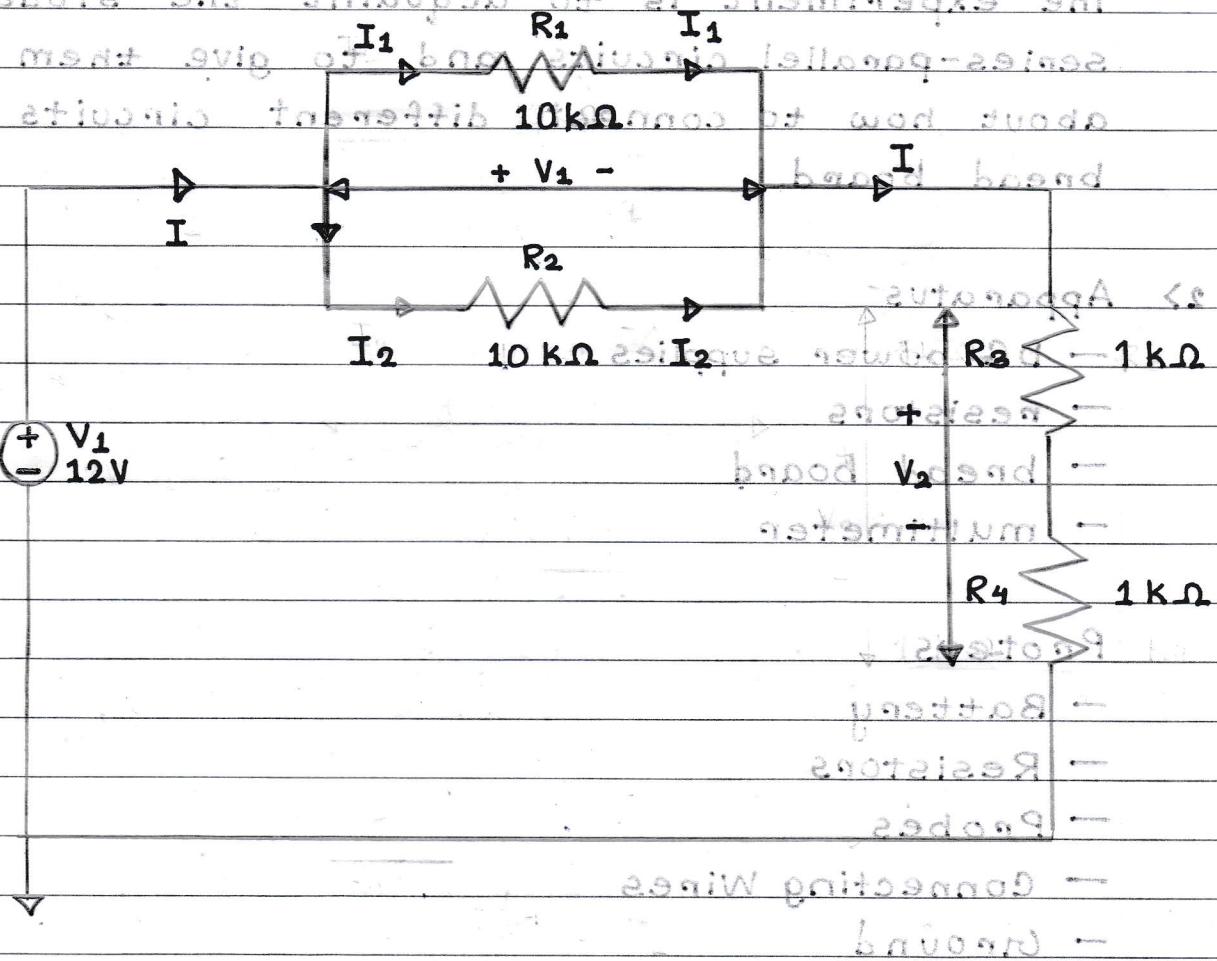
ai etiobis tneftib $10\text{ k}\Omega$ at wod zuodo



(b)

Results / Analyses

Currents (a)

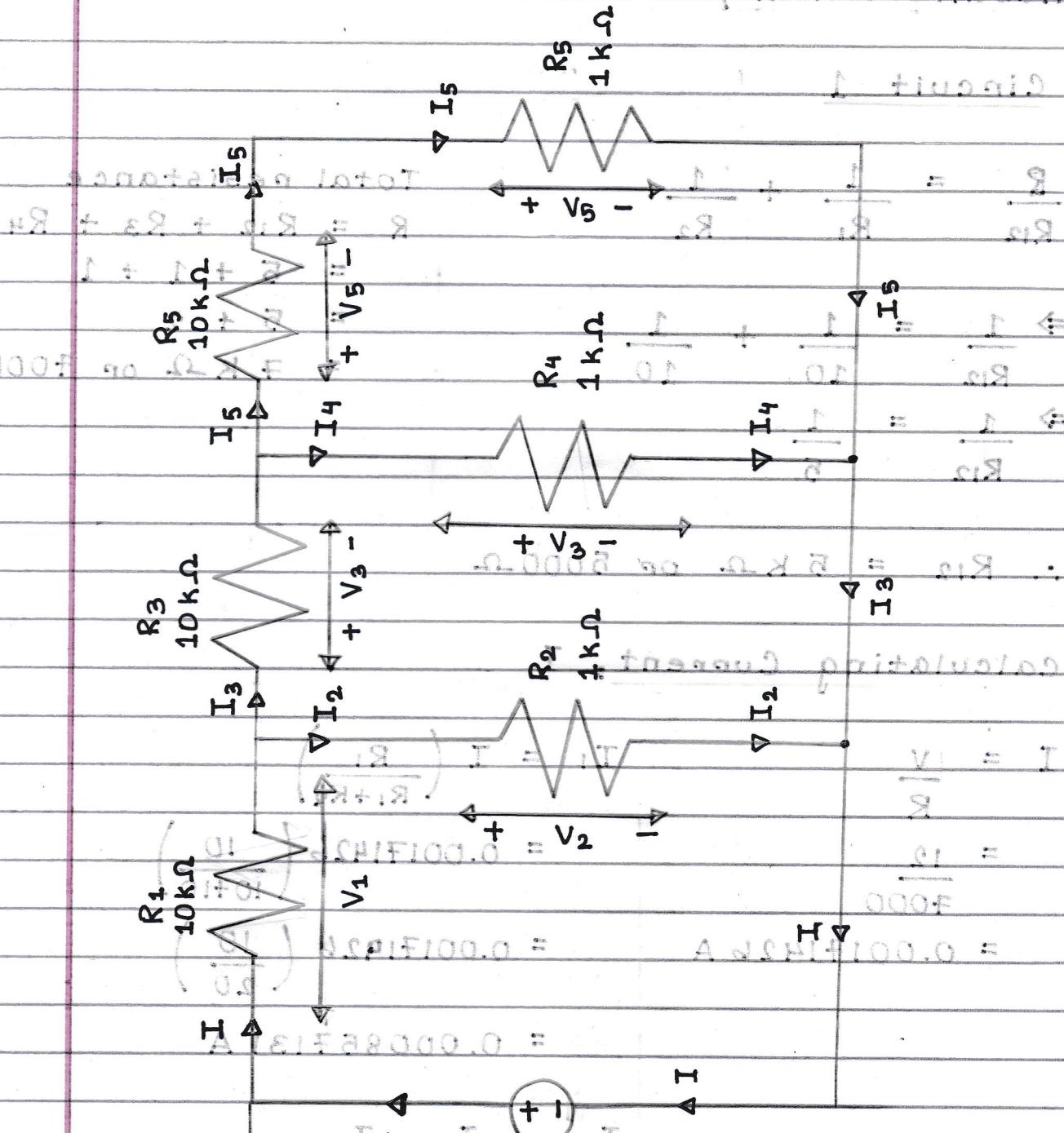

4) Results / Analysis

(a)

(a) Circuit 1

$$\frac{1}{R_{12}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\Rightarrow \frac{1}{R_{12}} = \frac{1}{10} + \frac{1}{10}$$

$$\Rightarrow \frac{1}{R_{12}} = \frac{1}{5}$$

$$\therefore R_{12} = 5 \text{ k}\Omega \text{ or } 5000 \Omega$$

Total resistance

$$R = R_{12} + R_3 + R_4$$

$$= 5 + 1 + 1$$

$$= 5 + 2$$

$$= 7 \text{ k}\Omega \text{ or } 7000 \Omega$$

Calculating Current

$$I = \frac{V}{R}$$

$$= \frac{12}{7000}$$

$$= 0.00171426 \text{ A}$$

$$I_1 = I \left(\frac{R_1}{R_1 + R_2} \right)$$

$$= 0.00171426 \left(\frac{10}{10+10} \right)$$

$$= 0.00171426 \left(\frac{10}{20} \right)$$

$$= 0.000857131 \text{ A}$$

$$I_2 = I - I_1$$

$$= 0.00171426 - 0.000857131$$

$$= 0.000857131 \text{ A}$$

Calculating Voltage

(d)

$$V = IR$$

$$\Rightarrow V_2 = I (R_3 + R_4)$$

$$\Rightarrow V_2 = 0.00171426 (1000 + 1000)$$

$$\therefore V_2 = 3.42852 \text{ V}$$

Results


CURRENT			VOLTAGE		
I ₁	I ₂	I ₃	V _s	V ₁	V ₂
0.00171426	0.000857131	0.000857131	12	12	3.42852

$$(b) \text{ Circuit } 2 \quad \frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$\frac{1}{R_{\text{eq}}} = \frac{1}{10k\Omega} + \frac{1}{1k\Omega}$$

Calculating Total Resistance, R_T
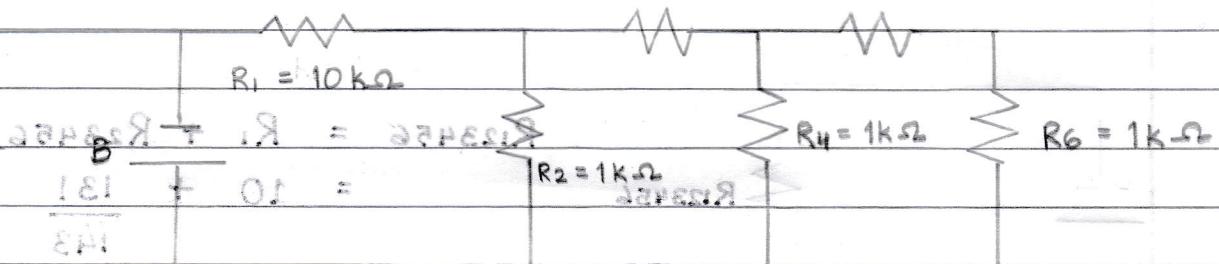
$$10k\Omega \parallel 1k\Omega = R_{\text{eq}}$$



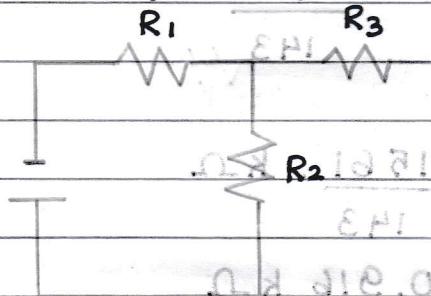
$$10k\Omega \parallel 1k\Omega = 1.25k\Omega$$



$$R_{56} = R_5 + R_6$$

$$= 10k\Omega + 1k\Omega \\ = 11k\Omega$$


$$10k\Omega \parallel 1.25k\Omega =$$

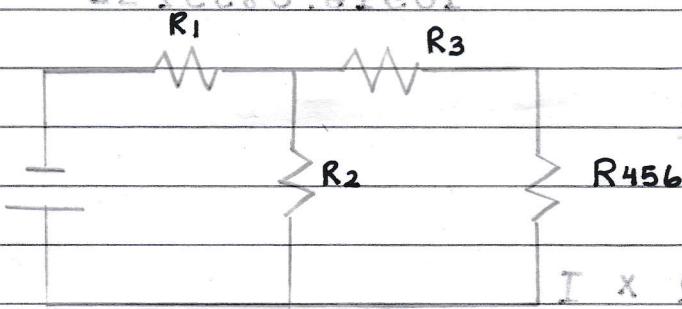

$$\frac{1}{R_{456}} = \frac{1}{R_4} + \frac{1}{R_5} \\ \Rightarrow \frac{1}{R_{456}} = \frac{1}{1} + \frac{1}{11} \\ \therefore R_{456} = \frac{11}{12} k\Omega$$


$$10k\Omega \parallel \frac{11}{12}k\Omega = 12 \Omega$$

$$A_{\text{diff}} = I$$

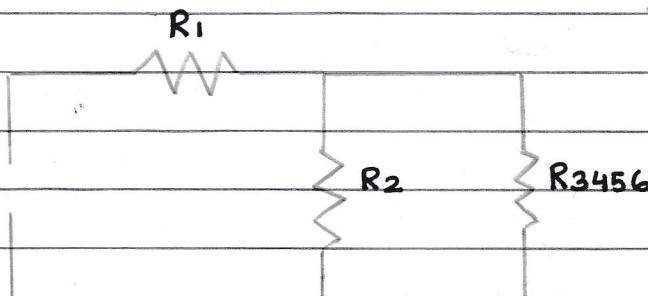

$$R_{3456} = R_3 + R_{456} \\ = 10 + \frac{11}{12} \\ = \frac{131}{12} k\Omega$$

$$= \frac{131}{12} k\Omega$$

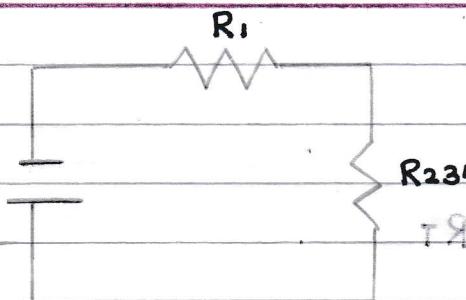


$$\frac{1}{R_{23456}} = \frac{1}{R_2} + \frac{1}{R_{3456}}$$

(d)

$$\Rightarrow \frac{1}{R_{23456}} = \frac{1}{10} + \frac{1}{\frac{131}{143}}$$
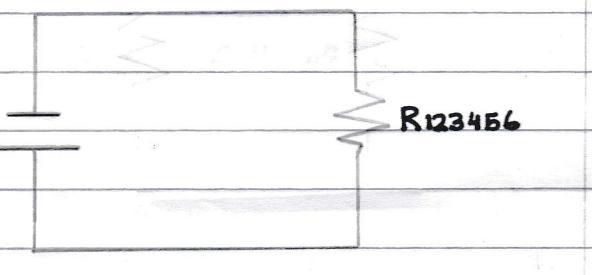
$$\therefore R_{23456} = \frac{131}{143} \text{ k}\Omega$$



$$R_{123456} = R_1 + R_{23456}$$

$$= 10 + \frac{131}{143}$$

$$= \frac{1561}{143} \text{ k}\Omega$$

$$R_1 + R_{23456} = R_{123456}$$

~~$$\text{Total resistance, } R_T \Rightarrow \frac{1561}{143} \text{ k}\Omega$$~~

~~$$R_T = \dots$$~~

~~$$= 10.916$$~~

~~$$= \underline{\underline{10916.08392 \Omega}}$$~~

Calculating Current

$$\frac{V}{R_1} + \frac{V}{R_{123456}} = \frac{V}{R_T}$$

$$\therefore V = IR$$

$$\Rightarrow 12 = 10916.08392 \times I$$


$$\therefore I = 1.099295 \text{ mA}$$

$$= \underline{\underline{1.10 \text{ mA}}}$$

$$R_1 + R_{23456} = R_{123456}$$

$$\frac{1}{R_1} + \frac{1}{R_{123456}} = \frac{1}{R_T}$$
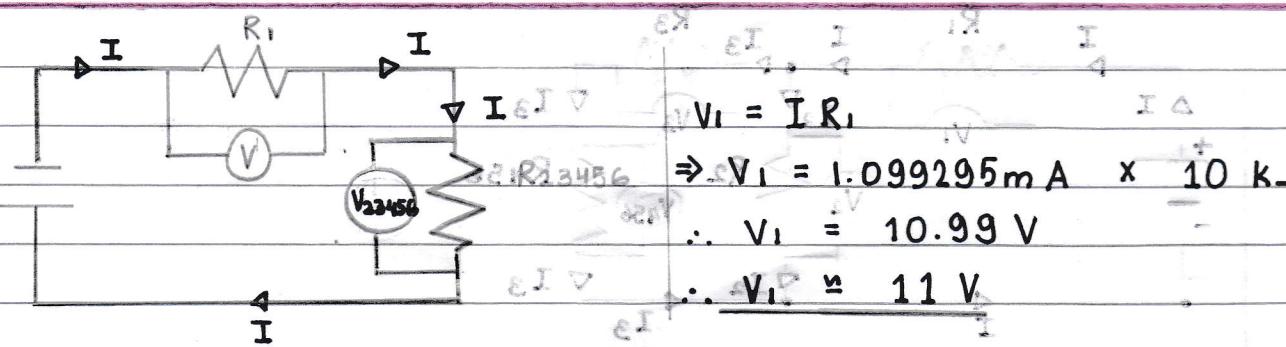
$$\frac{1}{R_1} + \frac{131}{143} = \frac{1}{R_T}$$



$$V_1 = IR_1$$

$$\Rightarrow V_1 = 1.099295 \text{ mA} \times 10 \text{ k}\Omega$$

$$\therefore V_1 = 10.99 \text{ V}$$

$$\therefore V_1 \approx 11 \text{ V}$$

$$V_{23456} = 12I - V_1$$


$$IR_1 = 6 \text{ V}$$

$$12I = 12 - 10.99$$

$$IR_2 = 6 \text{ V}$$

$$12I = 1.01 \text{ V} \Leftarrow 12 \text{ mA} \times 100 \text{ k}\Omega = 1.01 \text{ V} \Leftarrow$$

$$V_{23456} = 6 \text{ V} \therefore$$

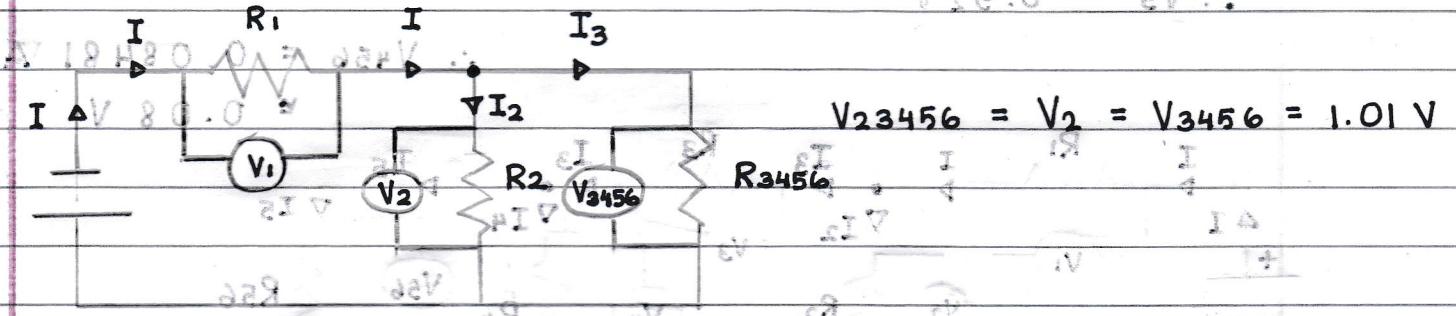

$$\therefore V_2 = 1.01 \text{ V}$$

$$V = IR$$

$$\Rightarrow V_{3456} = I_3 R_{3456}$$

$$V = IR$$

$$\Rightarrow 8.01 = I_3 \left(\frac{131}{12} \times 1000 \right)$$

$$\Rightarrow V_2 = I_2 R_2$$

$$\Rightarrow 1.01 = I_2 (1) \therefore I_3 = 9.2519084 \times 10^{-5} \text{ A}$$

$$\therefore I_2 = 1.01 \text{ mA} \Leftarrow$$

$$= 0.092528 \text{ mA} = 92.528 \mu\text{A} \Leftarrow$$

$$0.0001 \times 1.01 \times 10^3 = 1.01 \text{ V} \Leftarrow \therefore I_3 = 0.092528 \text{ mA} = 92.528 \mu\text{A} \Leftarrow$$

$$A \times 10^{-3} \times 10^3 = 1.01 \text{ V} \therefore$$


$$A \times 10^{-3} \times 10^3 = 1.01 \text{ V} \therefore$$

$$A \times 10^{-3} \times 10^3 = 1.01 \text{ V} \therefore$$

$$A \times 10^{-3} \times 10^3 = 1.01 \text{ V} \therefore$$

$$10.0 =$$

$$0.092528 \text{ mA} \Leftarrow$$

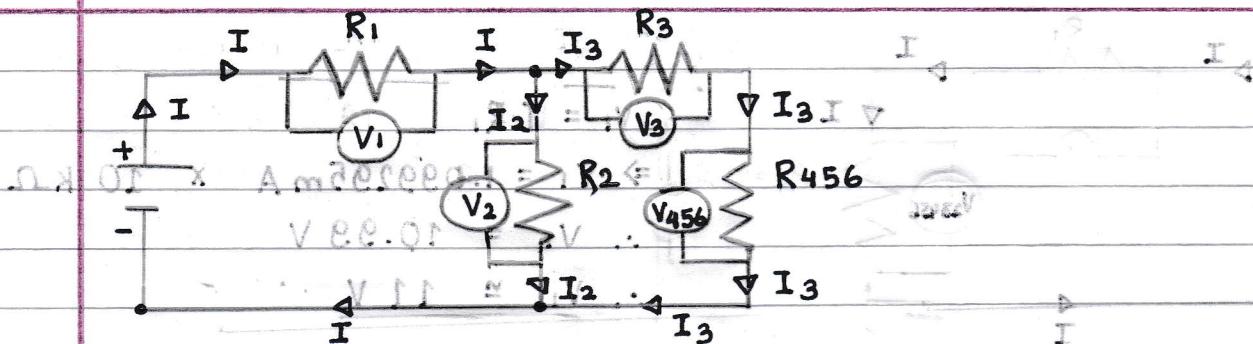

$$V_3 = IR$$

$$\Rightarrow V_3 = I_3 R_3$$

$$\Rightarrow V_3 = 0.09252 \text{ mA} \times 10 \text{ k}\Omega \Rightarrow V_{456} = 0.09252 \times \frac{11}{12}$$


$$\therefore \underline{V_3 = 0.92 \text{ V}}$$

$$VV = -IR = -0.92 \text{ V}$$

$$\Rightarrow V_{456} = I_3 R_{456}$$

$$\therefore \underline{V_{456} = 0.08481 \text{ V}} \\ \approx 0.08 \text{ V}$$
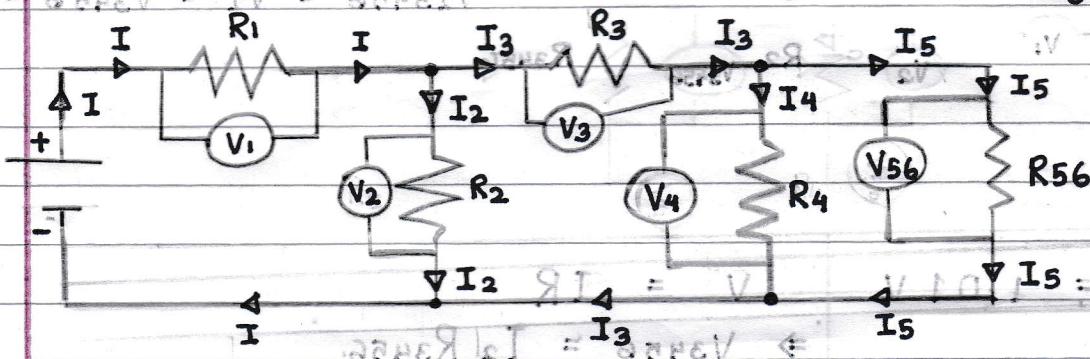
$$V_{10.1} = 0.92 \text{ V} = V = 0.92 \text{ V}$$



$$V_{400} = V_{56} = V_{456} = 0.08 \text{ V}$$

$$RI = V$$

$$RI = 0.08 \text{ V} \Leftrightarrow$$

$$V = IR \Leftrightarrow 0.08 = I R \Leftrightarrow$$

$$V = (IR) \Leftrightarrow 0.08 = (I R) \Leftrightarrow$$

$$\Rightarrow V_4 = I_4 R_4 \Leftrightarrow 0.08 =$$

$$V_56 = I_5 R_{56} \Leftrightarrow$$

$$\Rightarrow 0.08 = I_4 (10 \times 1000) \Leftrightarrow$$

$$\Rightarrow 0.08 = I_5 \times 11 \times 1000$$

$$\therefore I_4 = 8 \times 10^{-5} \text{ A}$$


$$\therefore I_5 = 7.7099 \times 10^{-6} \text{ A}$$

$$\therefore \underline{I_4 = 0.08 \text{ mA}}$$

$$= 7.7099 \times 10^{-3} \text{ mA}$$

$$= 0.07$$
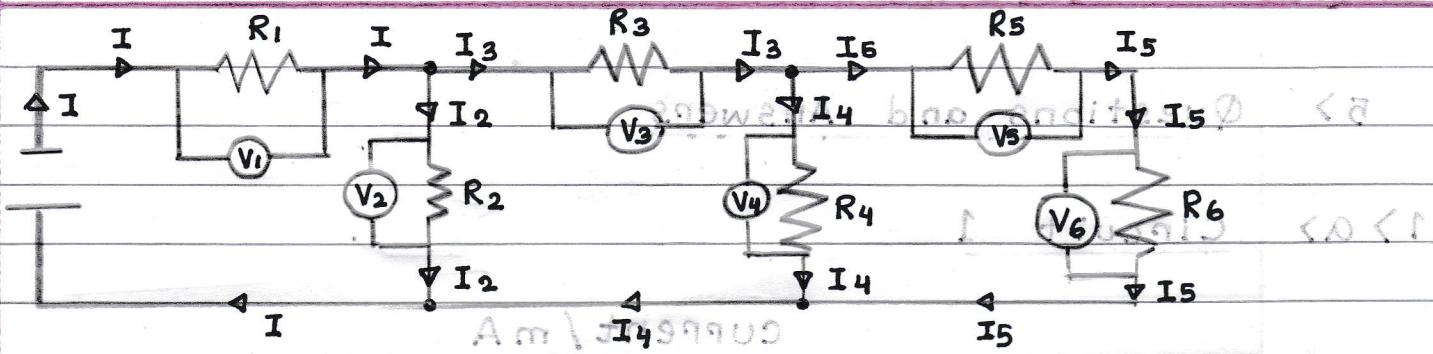
$$\therefore \underline{I_5 \approx 7.69 \mu\text{A}}$$



$$V_5 = I_5 R_5$$

$$= 7.69 \times 10^{-3} \text{ mA} \times 10 \text{ k}\Omega$$

$$\therefore V_5 = 0.0769 \text{ V}$$

$$V_6 = I_5 R_6$$

$$= 7.69 \times 10^{-3} \text{ mA} \times 1 \text{ k}\Omega$$

$$\therefore V_6 = 7.69 \times 10^{-3} \text{ V}$$

Results

current / mA					voltage / V						
I	I_2	I_3	I_4	I_5	I_6	V_1	V_2	V_3	V_4	V_5	V_6
1.10	1.01	0.09	0.08	7.69×10^{-3}	11	1.01	0.92	0.08	0.0769	7.69×10^{-3}	

± 0.1% e.s.f. 80.0 0.0 10.1 10.1

5 > Questions and Answers

1 > a) Circuit 1


	current / mA	
I	$0.8 \times 10^{-3} A = 0.8 \text{ mA}$	$\therefore I_2 = 0.8 \text{ mA}$
1. 7143	0.8571	0.8571 mA
		0.8571 mA

b) circuit 2


v	v	v	v	v	v	v	v	v	v	v	v
I	I_2	I_3	I_4	I_5	I_6	I_7	I_8	I_9	I_{10}	I_{11}	I_{12}
1.01	1.01	0.09	0.08	7.69×10^{-3}							

4>

Diagrams <

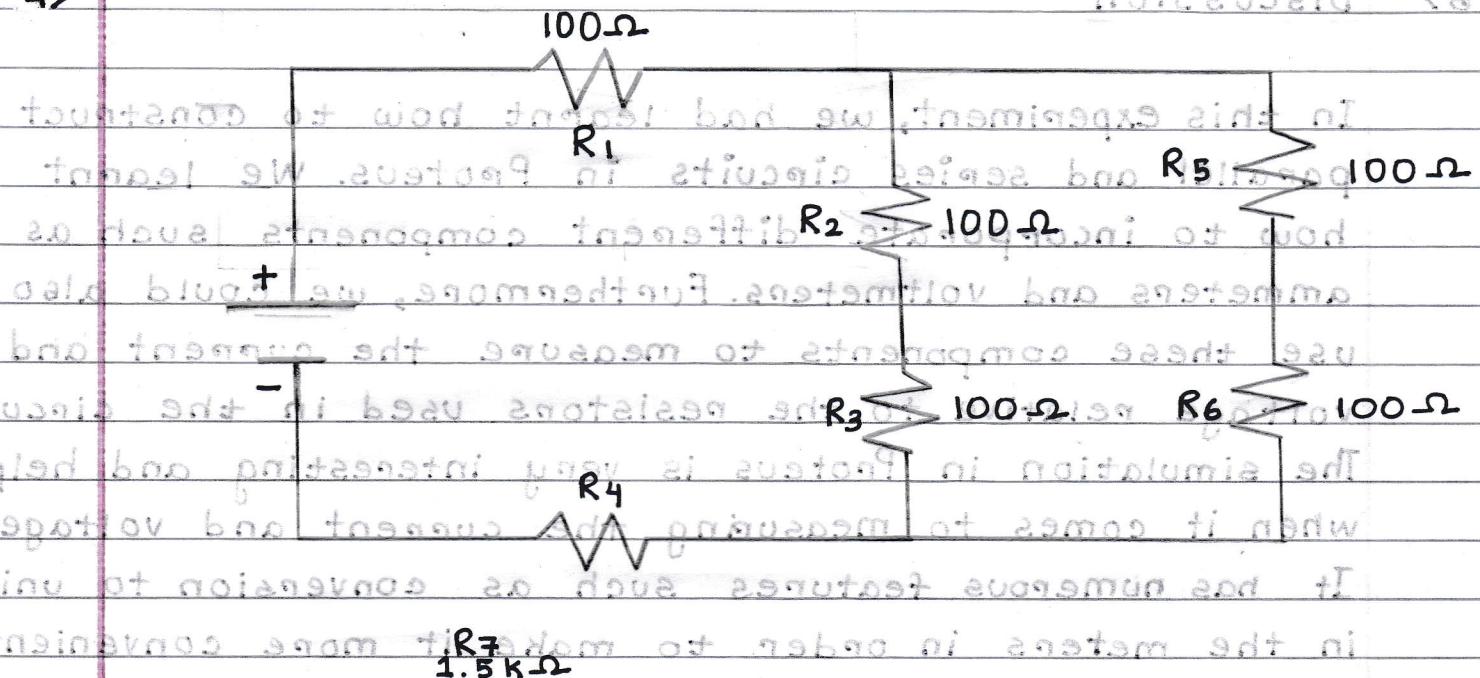

5>

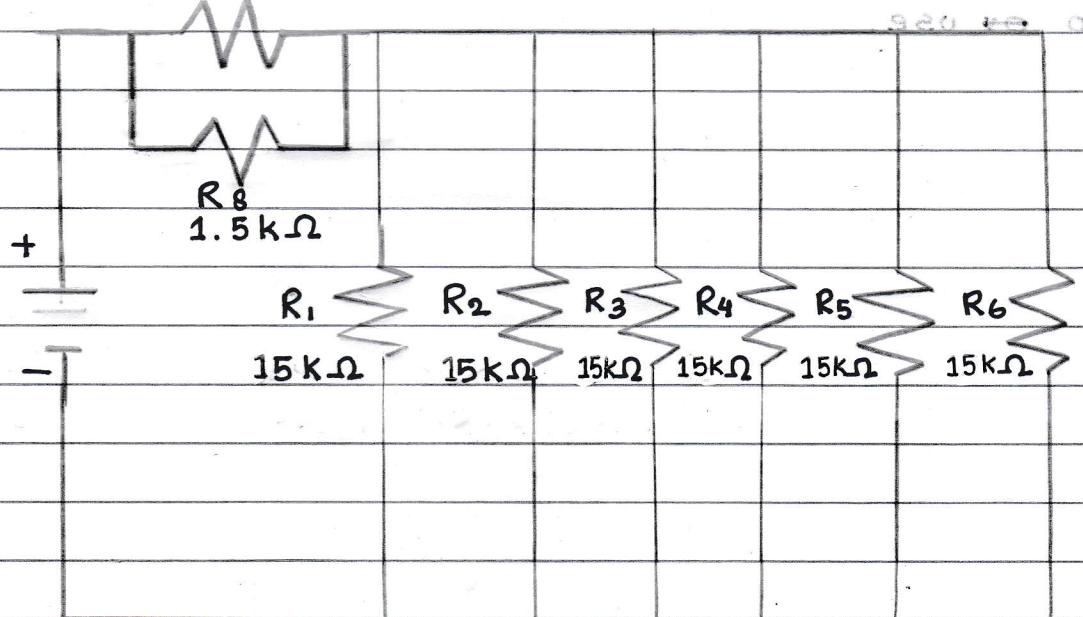


6> Discussion


15

In this experiment, we had learnt how to construct parallel and series circuits in Proteus. We learnt how to incorporate different components such as ammeters and voltmeters. Furthermore, we could also use these components to measure the current and voltage relative to the resistors used in the circuit. The simulation in Proteus is very interesting and helpful when it comes to measuring the current and voltage. It has numerous features such as conversion to units in the meters in order to make it more convenient to use.

14

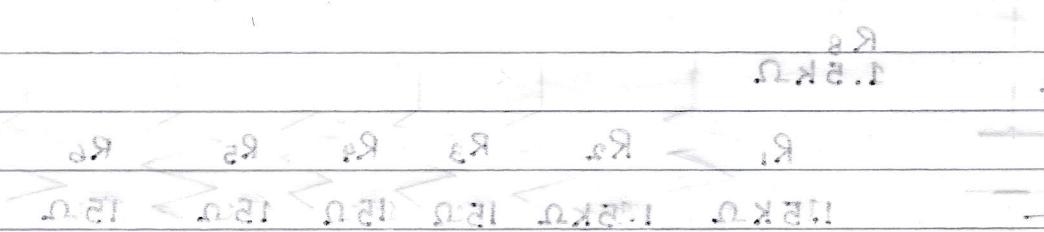

(a)

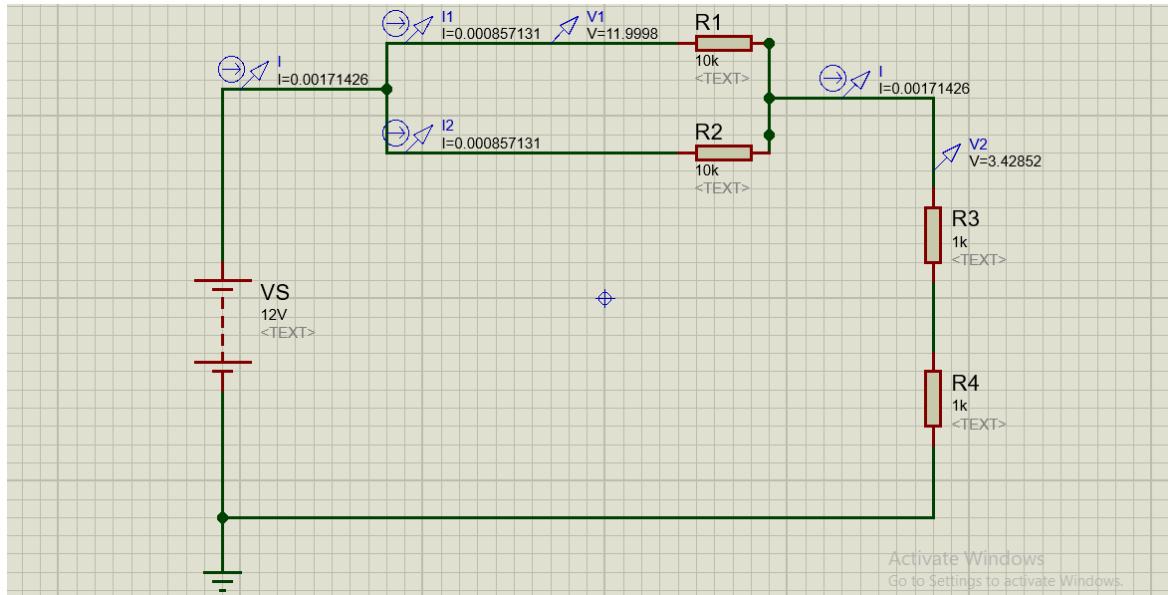

(b)

