

CSE350


DIGITAL ELECTRONICS AND PULSE TECHNIQUES

LAB ASSIGNMENT 06


SHAIANE PREMA BAROI

ID: 21101098


SECTION: 10

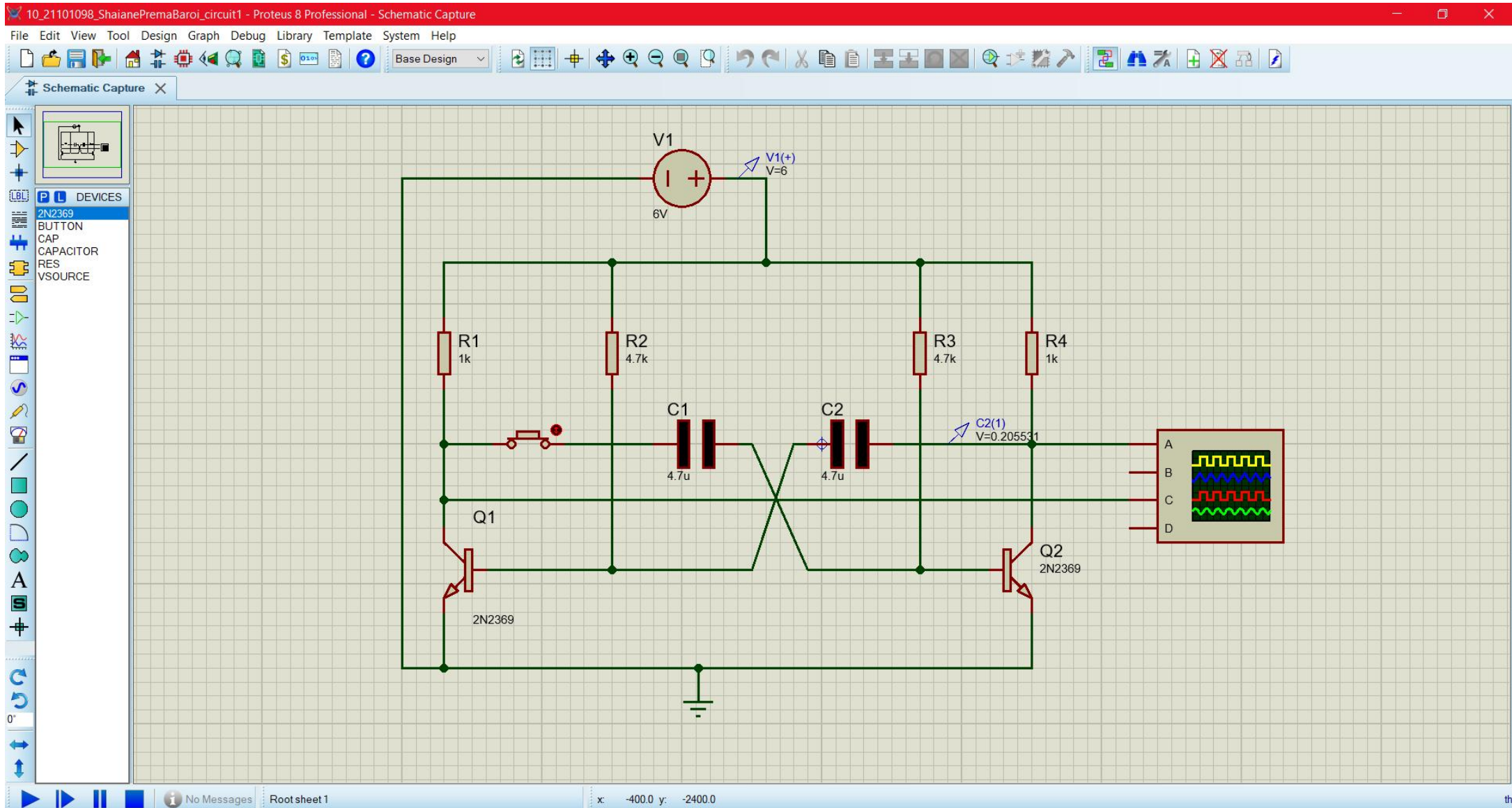

Digital Oscilloscope

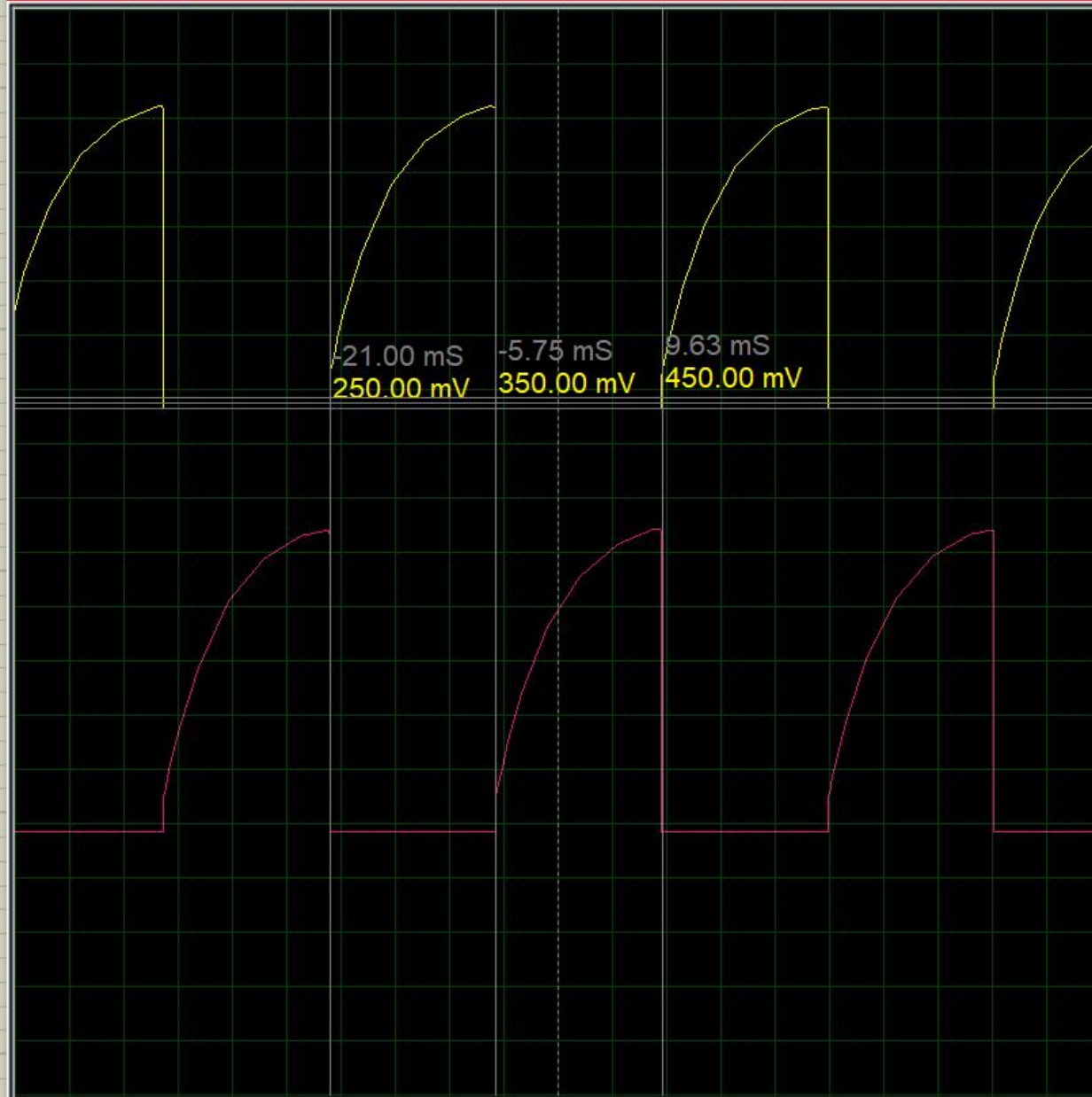

Trigger

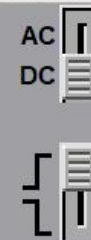



Auto
One-Shot
Cursors

Source



Channel A

Position

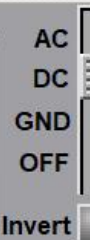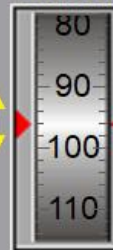

Invert

A+B



V 1 mV


Channel C

Position



Invert

A+B

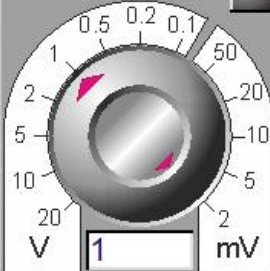

V 1 mV

Horizontal

Source





Position



mS 5m MS

Channel B

Position

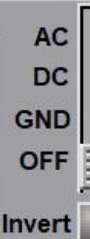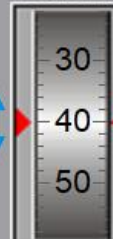

Invert


A+B



V 5 mV


Channel D

Position

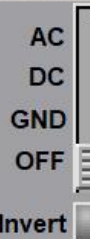

Invert

A+B

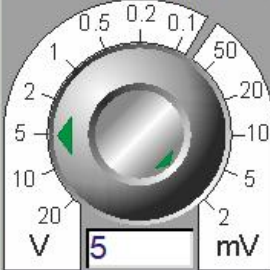


V 5 mV


Report

1. output waveforms

Channel A

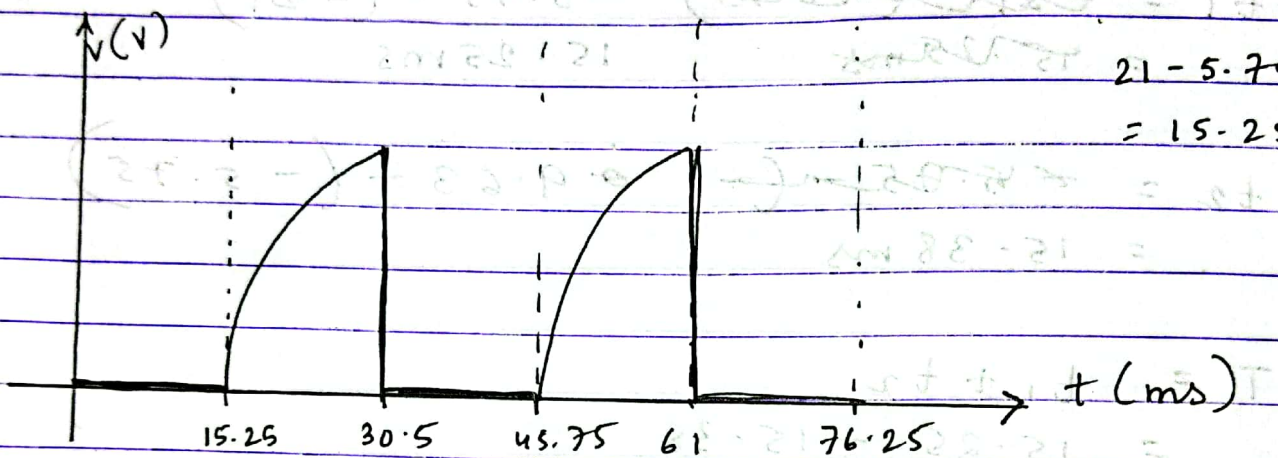

Channel B C

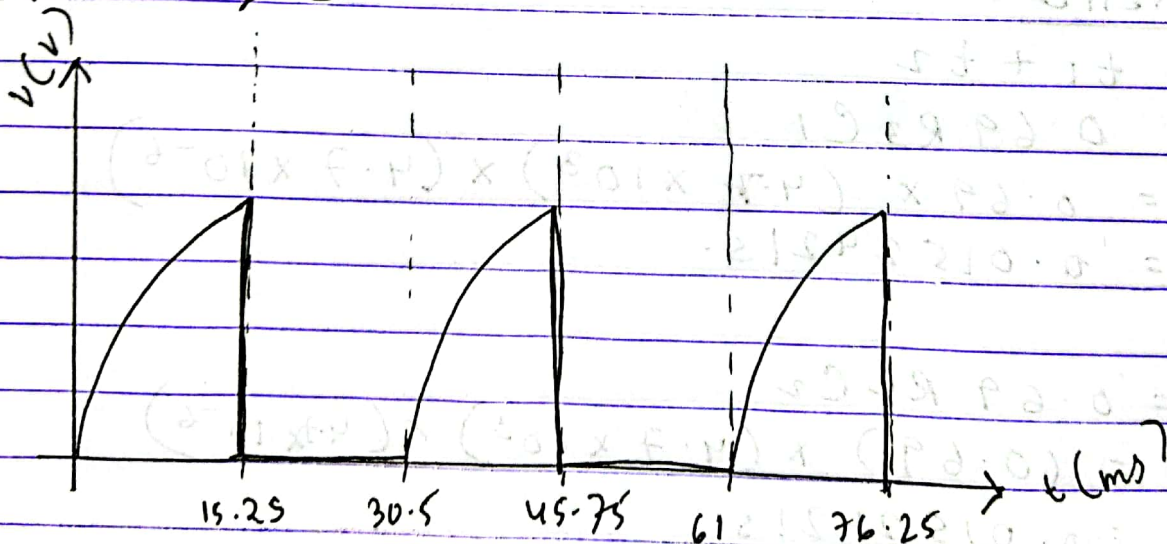

- 2) Yes, there is significant deviation. This is because in the experiment, the capacitor requires time to charge and discharge, hence its curve is more curved.

Experimental

$$3) \quad t_1 = \frac{-5.75 - (-21)}{15.25 \text{ ms}} = 15.25 \text{ ms}$$

$$t_2 = \frac{9.63 - (-5.75)}{15.38 \text{ ms}} = 15.38 \text{ ms}$$

$$T = t_1 + t_2 \\ = 15.25 + 15.38 \\ = 30.63 \text{ ms}$$

Theoretical

$$T = t_1 + t_2$$

$$t_1 = 0.69 R_3 C_1 \\ = 0.69 \times (4.7 \times 10^3) \times (4.7 \times 10^{-6}) \\ = 0.0152421 \text{ s}$$

$$t_2 = 0.69 R_2 C_2 \\ = (0.69) \times (4.7 \times 10^3) \times (4.7 \times 10^{-6}) \\ = 0.0152421 \text{ s}$$

$$T = t_1 + t_2 = 0.0152421 \times 2 = 0.03048 = 30.48 \text{ ms}$$

\therefore Yes time periods are similar.

4. Yes it is possible if the frequency is changed using the capacitors or resistors

$$T = 0.69R_3C_1 + 0.69R_2C_2$$

$$f = \frac{1}{t} = \frac{1}{0.69R_3C_1 + 0.69R_2C_2}$$

5. Duty cycle = $\frac{0.69R_3C_1}{0.69R_3C_1 + 0.69R_2C_2}$

$$= \frac{0.69(4.7)(4.7)}{0.69(4.7)(4.7) + 0.69(4.7)(4.7)}$$

$$= 50\%$$

So, duty cycle can be changed using capacitors or resistors.