

CSE260 Lab Report

Experiment Name: Applications of Kmap method

Submitted by

Name: Shaiane Prema Baroi

ID: 19241019

Section: 05

Date: 29 / 11 / 2020

1> Name of the Experiment : Applications of Kmap method


2> Objective :

- to investigate the rules of kmap
- to gain experience working with practical circuits
- to simplify a complex function using kmap


3> Required Components and Equipments

- AT-100 Portable Analog / Digital Laboratory
- AND, OR, NOT, XOR IC
- LOGIC PROBE (BIL)
- LOGIC STATE
- WIRES

4> Experimental Setup

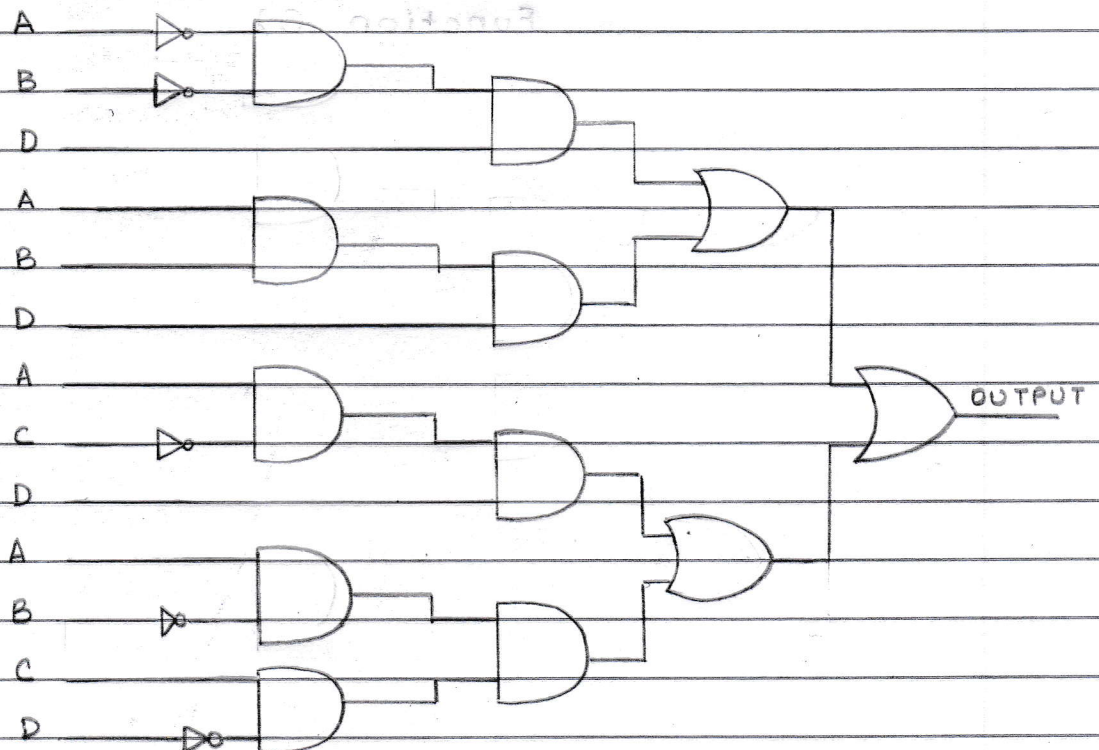

Function 01

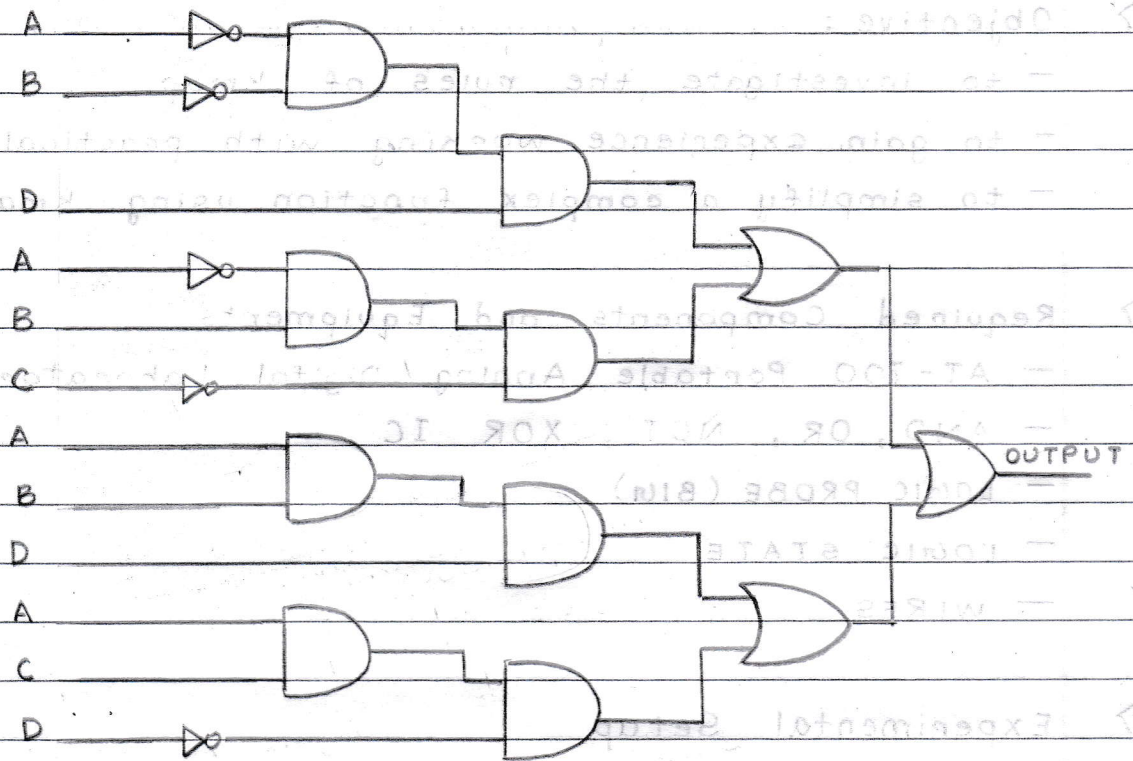

Function 02

5) Results and Discussions

$$1. F(A, B, C, D) = \sum (1, 3, 9, 10, 13, 15)$$

	$C'D'$	$C'D$	CD	CD'
$A'B'$	0	1	3	2
$A'B$	4	5	7	6
AB	12	13	15	14
AB'	8	9	11	10

$$\text{Answer} = A'B'D + ABD + AC'D + AB'CD'$$

$$2. F(A, B, C, D) = \sum (1, 4, 10, 15) + d(3, 13, 5, 14)$$

$A'B'$	$C'D'$	$C'D$	CD	CD'
0	1	X	3	2
4	X	5	7	6
12	X	13	15	X
8	9	11	10	14

$$\text{Answer} = A'B'D + A'BC' + ABD + ACD'$$

1

INPUTS

OUTPUTS

A

B

C

D

0

0

0

0

0

0

0

0

1

1

0

0

1

0

0

0

0

1

1

1

0

1

0

0

0

0

1

0

1

0

0

1

1

0

0

0

1

1

1

0

1

0

0

0

0

1

0

0

1

1

1

0

1

0

1

1

0

1

1

0

1

1

0

0

0

1

1

0

1

1

1

1

1

0

0

1

1

1

1

1

2.

INPUTS

OUTPUTS

A

B

C

D

0

0

0

0

0

0

0

0

1

1

0

0

1

0

0

0

0

1

1

1

0

1

0

0

1

0

1

0

1

1

0

1

1

0

0

0

1

1

1

0

1

0

0

0

0

1

0

0

1

0

1

0

1

0

1

1

0

1

1

0

1

1

0

0

0

1

1

0

1

1

1

1

1

0

1

1

1

1

1

1

Discussion

In this experiment, we had learnt how to construct a circuit from a given circuit by using K-map. At first, the task at hand seemed quite complicated to me. Even though I had a clear concept and understanding behind the idea of K-map, it took me some time to visualise how to use the simplified expression to construct the circuit. Then, I decided to take one step at a time, and started to evaluate the function into a simplified expression using the K-map. After I had obtained the simplified expression, I constructed the circuit using AND gates ~~and~~, OR gates and NOT gates in place of dots, pluses and primes respectively. As a result, I obtained two circuits for two functions. However, one silly problem which I faced during the experiment was that I did not connect two close components with wires. I just placed them side by side, thinking that the components were connected. It took me quite some time to realise the roots of the errors which I receiving. Once, I had secured the connections with wines, I obtained accurate results and concluded the experiment successfully.