

21101098

CSE350

DIGITAL ELECTRONICS AND PULSE TECHNIQUES

LAB ASSIGNMENT 05


SHAIANE PREMA BAROI

ID: 21101098


SECTION: 10

Report

motorcycle circuit

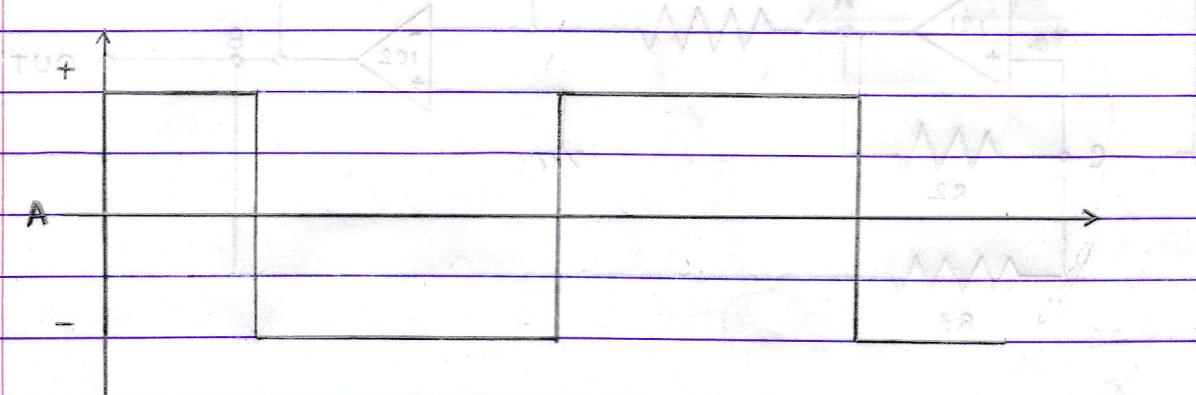1. Output wave shape at point A

output wave shape at point B

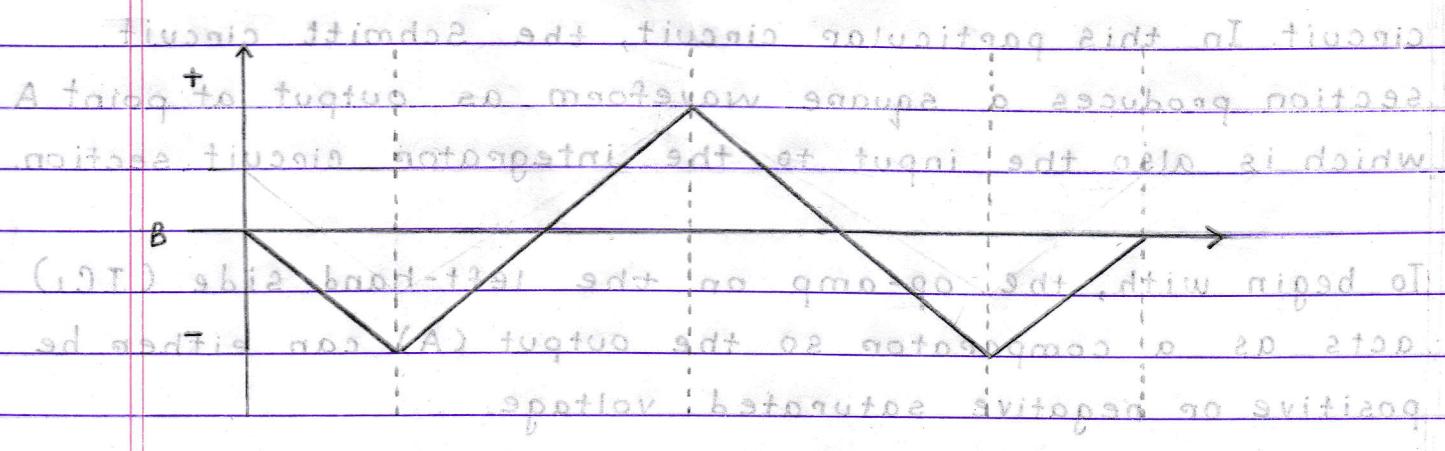


TAzV → TAzV ← A

points at node A and node B are connected to ground. The voltage at node A is 10V and the voltage at node B is 5V. The voltage at node C is 15V.

$$\Delta V = v_V = 10V$$

2. Circuit Operation

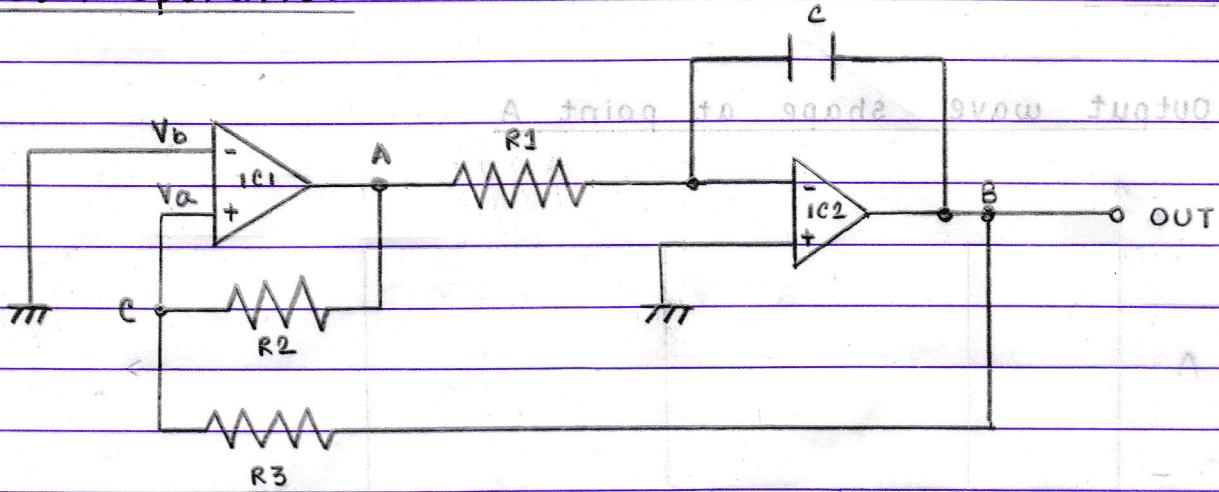

The triangular wave oscillator consists of two sections: a comparator circuit (Schmitt circuit) and an integrator circuit. In this particular circuit, the Schmitt circuit section produces a square waveform as output at point A which is also the input to the integrator circuit section.

To begin with, the op-amp on the left-hand side (IC₁) acts as a comparator so the output (A) can either be positive or negative saturated voltage.

$$A \rightarrow V_{SAT} \text{ or } -V_{SAT}$$

The difference between the voltage at the non-inverting terminal and the voltage at the inverting terminal can be defined as -

$$V_{id} = V_a - V_b$$

The voltage at the inverting terminal is connected to the ground, therefore -

$$V_b = 0$$

$$\Rightarrow V_{id} = V_a - 0 \text{ raaV = A } \text{ fi}$$

soptiony sdt = VO waled $\therefore V_{id} = V_a$ to soptiony bnt ngnw

sumim ofri zapproda (A) tisniaj ttimdab fo: tuatuq. sdt fo

sdt S6, when A) $V_a > 0$, then $V_{id} > 0$ and so $A = V_{sat}$

when $V_a < 0$, then $V_{id} < 0$ and so $B = -V_{sat}$

soit bao zasavas (C) natiogns sdt at wolt fnsqus

Hence, this is how a square waveform is produced at the output of the Schmitt circuit (A).

(A) tuatuq. sdt, VO abssys 3 tiaq to soptiony sdt ngnw

As mentioned before, the output (A) produced at the

Schmitt circuit (IC₁) is the input to the integrator

circuits (IC₂). So, when A is positive saturated voltage

(A = VSAT) then B is negative-going ramp. This is because

the electric current flows through the resistor (R₁) and

into the capacitor (C). Then, as the electric charge begins

to store up in the capacitor, voltage of the both edges


of the capacitor increases and so the voltage of the

output (B) of the integrator circuit (IC₂) decreases gradually

At the same time, the voltage at point C also decreases


when the voltage at point B also decreases.

qmon priop sv+ = a nent raaV = A fi

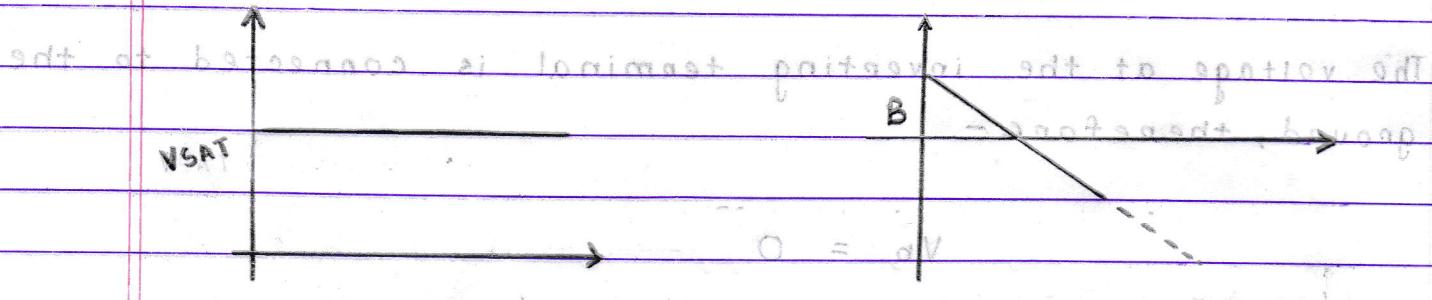

if $A = VSAT$ then $B = -ve$ going ramp

When the voltage at point C falls below OV, the voltage of the output of Schmitt circuit (A) changes into minus rapidly. When A is negative-saturated ($A = -VSAT$), then B is positive-going ramp. This is because the electric current flow to the capacitor (C) reverses and the electric current flows through the direction of point A through the resistor (R_1), the voltage of point B increases. When the voltage of point C exceeds OV, the output (A) of the Schmitt circuit changes into the plus rapidly. This process repeats and therefore, a square waveform is produced at the output of the Schmitt circuit (A) and a triangular waveform is produced at the output of the integrator circuit (B).

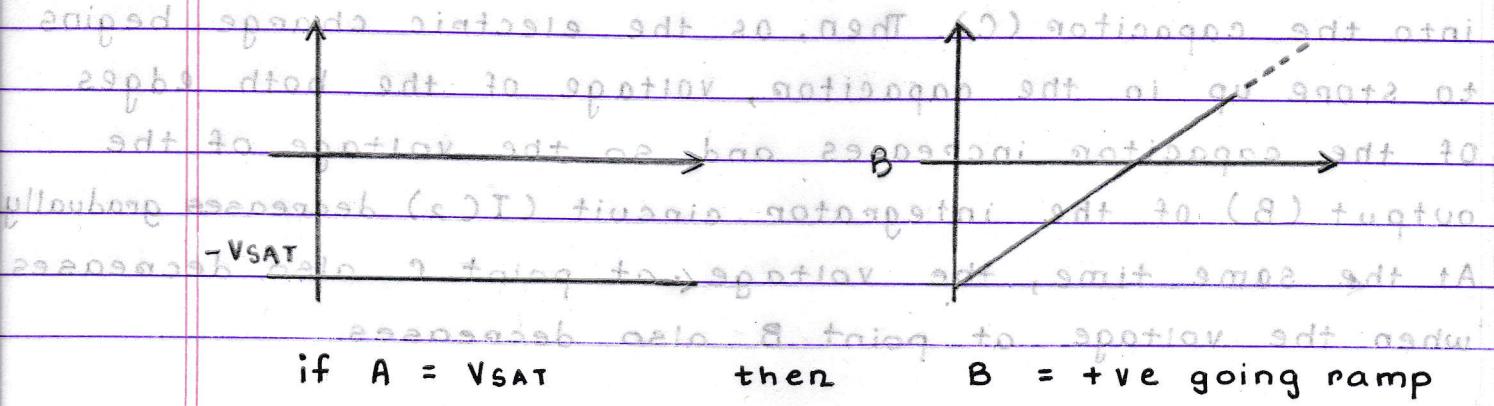


if $A = VSAT$ then $B = +ve$ going ramp

3.2.2.1 Yes, the integrator circuit can be implemented with an inductor.

op-amp input = iV

op-amp output = oV

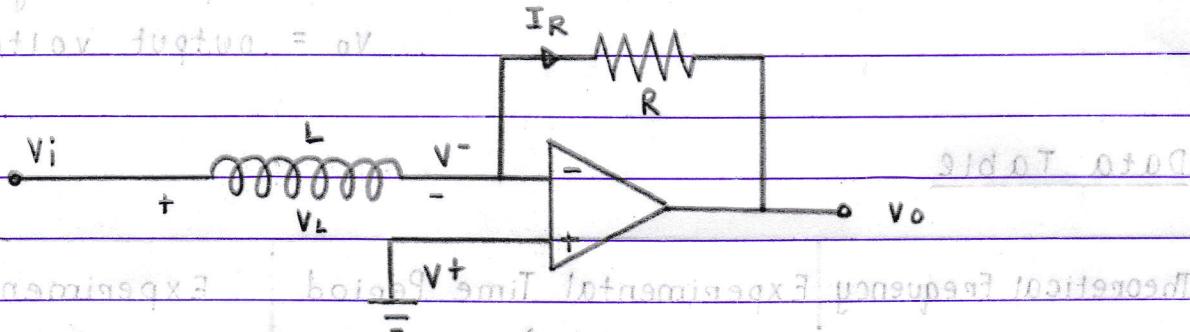

$$I_R = \frac{V_0 - V_o}{R} = -\frac{V_o}{R} \quad \left. \begin{array}{l} V^- = 0V \\ V^+ = 0V \end{array} \right\} \text{virtual ground concept}$$

$$\text{KCL} \quad I_L = 0 + I_R \times V_L = V_i - 0 \quad \left. \begin{array}{l} V_L = \frac{dI_L}{dt} \\ I_L = I_R \end{array} \right\} \therefore V_L = V_i$$

$$\therefore V_L = L \frac{dI_L}{dt} = L \frac{dI_R}{dt}$$

$$(L \frac{dI_R}{dt}) = -V_L = -L \frac{dV_o}{dt} \quad \left. \begin{array}{l} V_L = -L \frac{dV_o}{dt} \\ V_L = \frac{dV_o}{dt} \end{array} \right\} \text{virtual ground concept}$$

$$\Rightarrow -\frac{R}{L} V_i = \frac{dV_o}{dt}$$

$$\Rightarrow \int \frac{dV_o}{dt} dt = - \int \frac{R}{L} V_i dt$$

$V_o = \frac{R_f}{L} \int R_i V_i dt$ where, R_f = negative feedback resistance
 L = inductance
 V_i = input voltage
 V_o = output voltage

Data Table

| Theoretical Frequency | Experimental Time Period T (ms) | Experimental Frequency F (Hz) |
|-----------------------|------------------------------------|----------------------------------|
| 156.25 | 6.50 | 154 |
| | 6.50 | 154 |

$$\text{Theoretical frequency, } f = \frac{1}{4\pi C} \times \frac{R_2 + R_3}{R_1} = \frac{1}{(4 \times 10 \times 10^{-3} \times 0.4 \times 10^{-6})} \times \frac{10}{4} = 156.25 \text{ Hz}$$

$$\text{Experimental Time Period, } t = (6.48 \times 10^{-3}) - (12.98 \times 10^{-3}) = 6.50 \times 10^{-3} \text{ s} = 6.50 \text{ ms}$$

$$\text{Experimental frequency, } f = \frac{1}{t} = \frac{1}{6.50 \times 10^{-3}} = 153.8 \text{ Hz} \approx 154 \text{ Hz}$$

