

# CSE260 Lab Report

Experiment Name: IMPLEMENTATION OF 4-BIT MAGNITUDE  
COMPARATOR

Submitted by

Name: SHAIANE PREMA BAROI

ID: 19241019

Section: 05

Date: ~~11~~ / 12 / 2020  
27

1> Name of the experiment: Implementation of a 4-bit Magnitude Comparator

2> Objective: To design a circuit that will act as a Magnitude Comparator between two 4-bit numbers.

- draw a circuit that will act as a Magnitude Comparator between two 4-bit numbers
- implement the circuit

3> Required Components:

- AND gate
- OR gate
- NOR gate
- NOT gate
- LED light
- Logic States
- Ground
- Wires

4> Experimental Setup

- shown in Proteus file

## 57 Results and Discussion

- a)  $A = B$  is only possible when  $A$  and  $B$  are equal, such as  $A = 0000$  and  $B = 0000$  OR  $A = 1111$  and  $B = 1111$ .
- b)  $A > B$  only possible when one bit is greater than the other, such as
- $A = 0010$  ,  $B = 0000$
- c)  $A < B$  only possible when  $B$  is greater than  $A$ .

$$A = 0000 , B = 0010$$

To find  $A < B$  from  $A > B$  and  $A = B$ , we need to add a 2-input NOR gate between the output of  $A > B$  and  $A = B$ .