

CSE260 Lab Report

Experiment Name: DESIGN A CIRCUIT THAT OUTPUTS
2'S COMPLEMENT OF A 3-BIT
NUMBER USING ENCODER &
DECODER

Submitted by

Name: SHAIANE PREMA BAROI

ID: 19241019

Section: 05

Date: 20 / 12 / 2020

1> Name of the experiment : Design a circuit that outputs 2's complement of a 3 bit number using encoder and decoder.


2> Objective:

— to design and implement a circuit that outputs the 2's complement of a 3-bit number using encoder and decoder


3> Required components and equipments:

- 74LS138
- 74LS148
- LED GREEN
- LOGIC STATE
- GROUND
- POWER
- WIRES


4> Experimental Setup

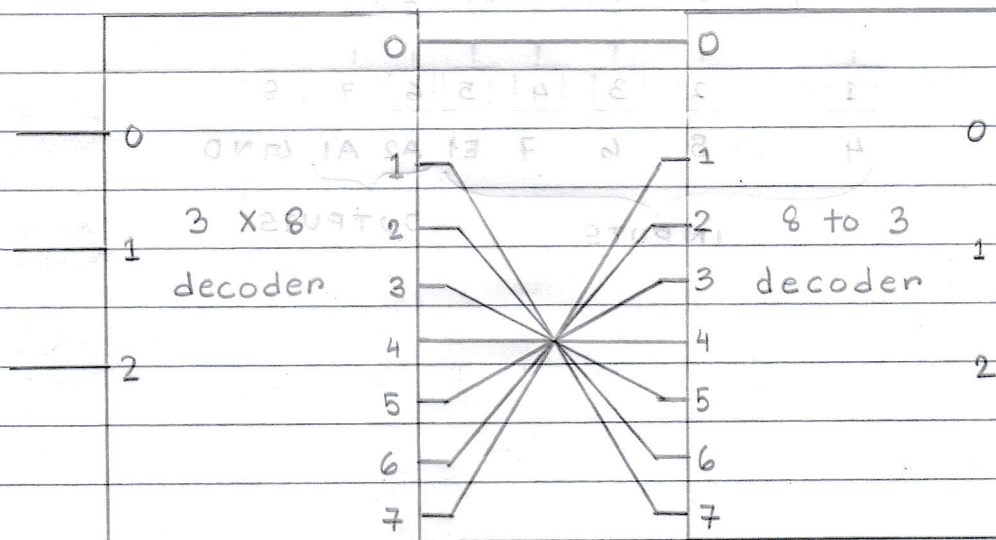

74138

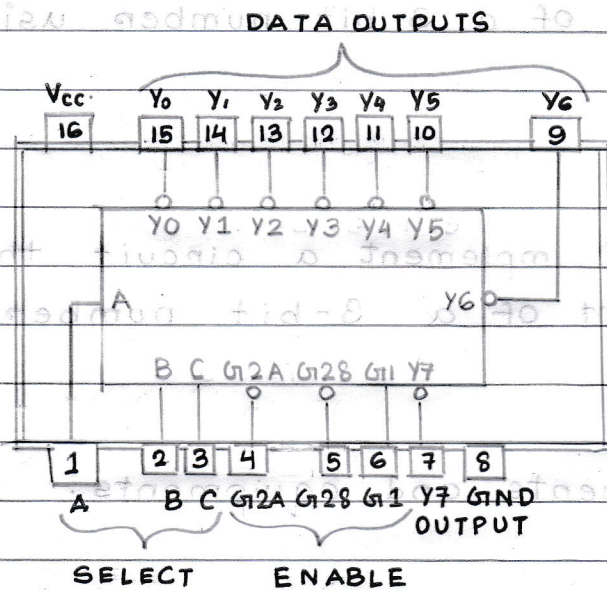


74148

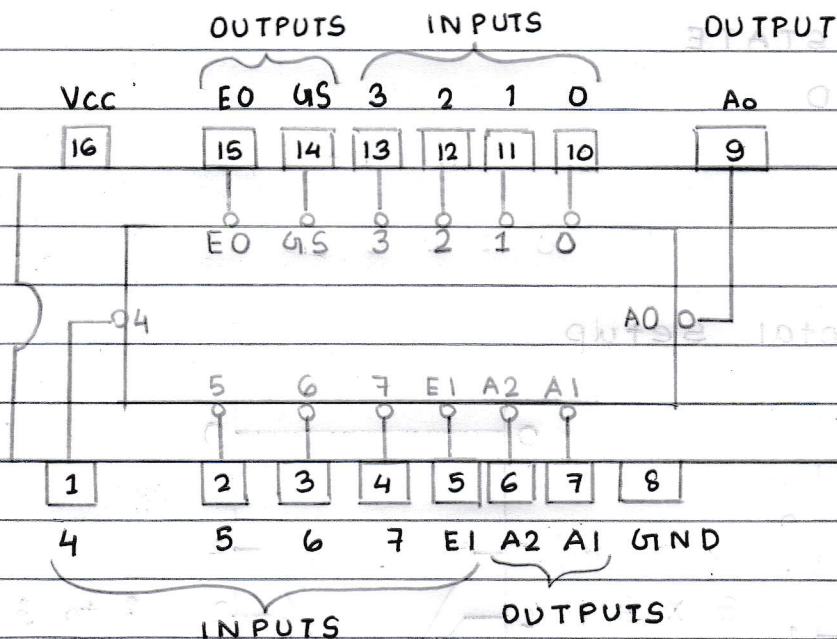

5> Results


Inputs				Outputs				Active Low Output			Output Line Connection	
Minterm	C	B	A	Minterm	D ₂	D ₁	D ₀	D ₂	D ₁	D ₀	Decoder	Encoder
0	0	0	0	0	0	0	0	1	1	1	0	0
1	0	0	1	7	1	1	1	0	0	0	1	7
2	0	1	0	6	1	1	0	0	0	1	2	6
3	0	1	1	5	1	0	1	0	1	0	3	5
4	1	0	0	4	1	0	0	0	1	1	4	4
5	1	0	1	3	0	1	1	1	0	0	5	3
6	1	1	0	2	0	1	0	1	0	1	6	2
7	1	1	1	1	0	0	1	1	1	0	7	1

a>

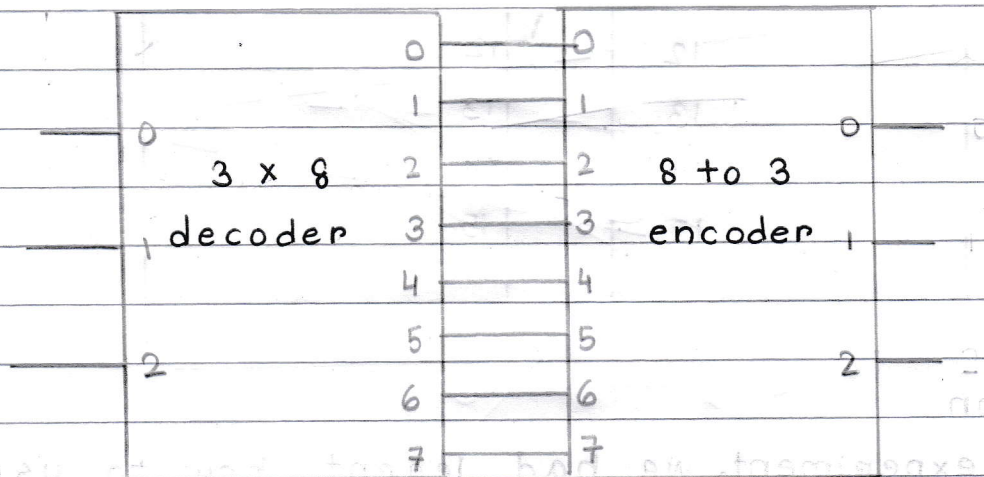

b> Yes, we can implement a code convertor with encoder and decoder. In this experiment, we had converted a binary number into 2's complement. Additionally, we had also designed and implemented a code converter in 5(a), where we converted a binary number (3-bit) into 1's complement number system. Similarly, we can also convert from BCD to excess-3

with the following circuit:

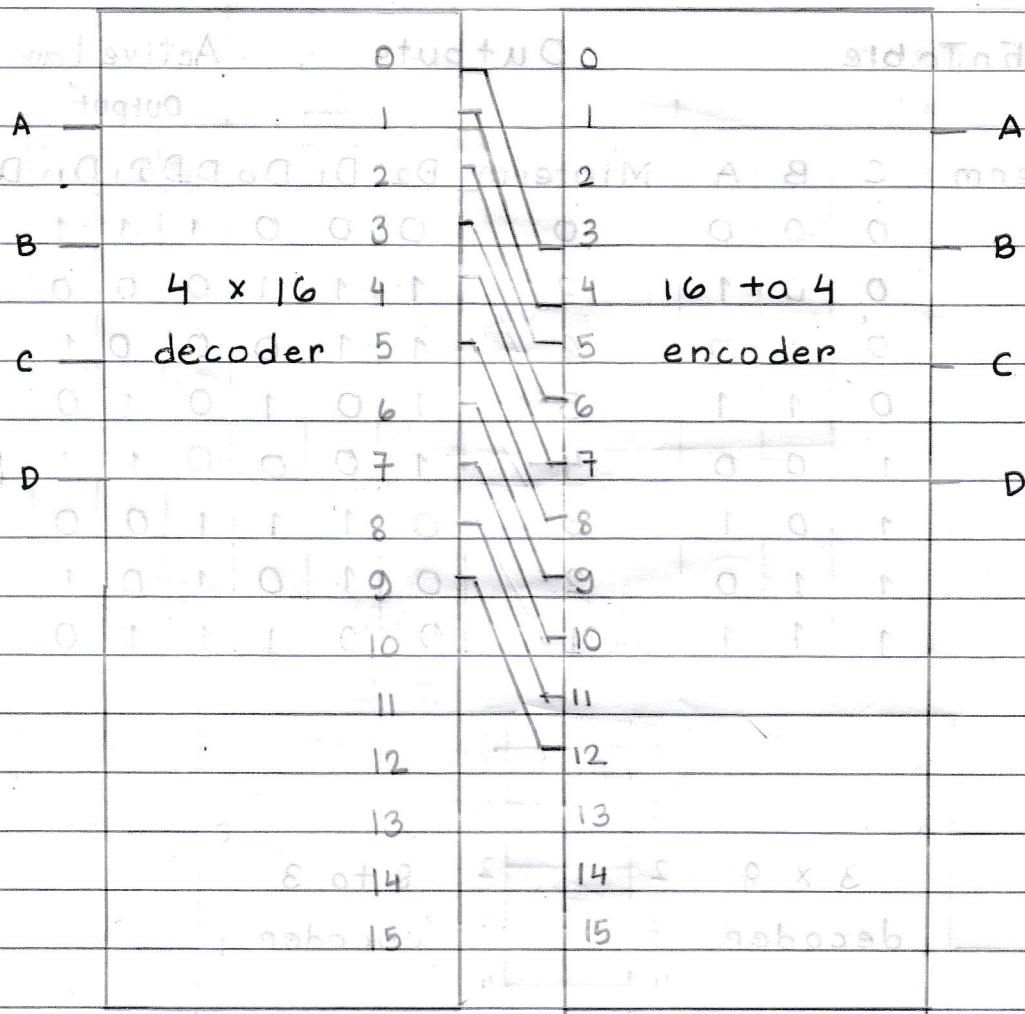

Discussion

In this experiment, we had learnt how to use different connections between decoders and encoders to convert an n -bit code from one form to another. Particularly, we had seen how to convert a 3-bit binary number to 2's complement number. Even though, the concept was a little difficult for me to grasp, however constructing the circuit was simple and easy to implement.